

Contents

1	Components	1
2	Connections	1
3	Problem	1
4	Truth table	1
5	Karnaugh-map	1
6	Code Link	1

1 Components

Component	Value	Quantity
Resistor	220 ohm	1
Arduino	UNO	1
Decoder	7447	1
Display		1
Bread board		1
Jumper wires	M-M	15

Table 1:

2 Connections

Make connections between Seven segment and 7447 IC as per table3.

7447	a'	b'	c'	d'	e'	f'	g'
Display	a	b	c	d	e	f	g

Table 2:


Make connections between Arduino and 7447 IC as per table4.

Arduino	2	3	4	5
7447	A	B	C	D

Table 3:

3 Problem

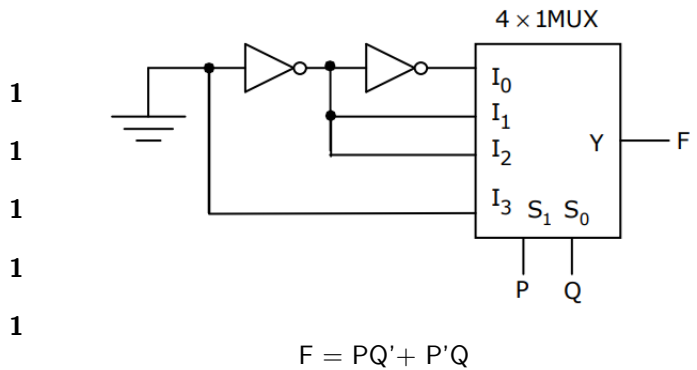The logic function implemented by the circuit given below is that of an XOR Gate



4 Truth table

P	Q	F
0	0	0
0	1	1
1	0	1
1	1	0

Table 4:

5 Karnaugh-map

		Q	
		0	1
P	0	0	1
	1	1	0

$$F = PQ' + P'Q$$

6 Code Link

Execute the following program to realize the Boolean logic for the given circuit
